

## Chapter 1

# Fundamental of Electrical Drives

**Professor Min-Fu Hsieh**

**Fall Semester - 2022**



<https://www.automationdirect.com/adc/overview/catalog/drives>



成功大學

National Cheng Kung University <sup>2</sup>

---

# Overview of Electrical Drives

Year

< 1950

## Before semiconductor devices were introduced

- AC motors for fixed speed applications
- DC motors for variable speed applications

1960s

## After semiconductor devices were introduced

- Variable frequency sources available – AC motors in variable speed applications
  - ✓ *Coupling between flux and torque control*
  - ✓ *Application limited to medium performance applications – fans, blowers, compressors – scalar control*
- High performance applications dominated by DC motors – tractions, elevators, servos, etc

1980s

## After vector control drives were introduced

- AC motors used in high performance applications – elevators, tractions, servos
- AC motors favorable than DC motors – however control is complex hence expensive
- Cost of microprocessor/semiconductors decreasing –predicted 30 years later AC motors would take over DC motors

# What is an AC Drive?

- A **variable-frequency drive (VFD)**; also termed adjustable-frequency drive, “variable-voltage/variable-frequency (VVVF) drive”, variable speed drive, **AC drive**, micro drive or inverter drive) is a type of adjustable-speed drive used in electro-mechanical drive systems to **control AC motor speed and torque** by varying motor **input frequency and voltage**.
- VFDs are made in a number of different low- and medium-voltage **AC-AC** and **DC-AC** topologies.



*Small variable-frequency drive*




*Inside of VFD (cover removed)*

- [https://en.wikipedia.org/wiki/Variable-frequency\\_drive](https://en.wikipedia.org/wiki/Variable-frequency_drive)


# An Actual AC Drive (VFD)

5

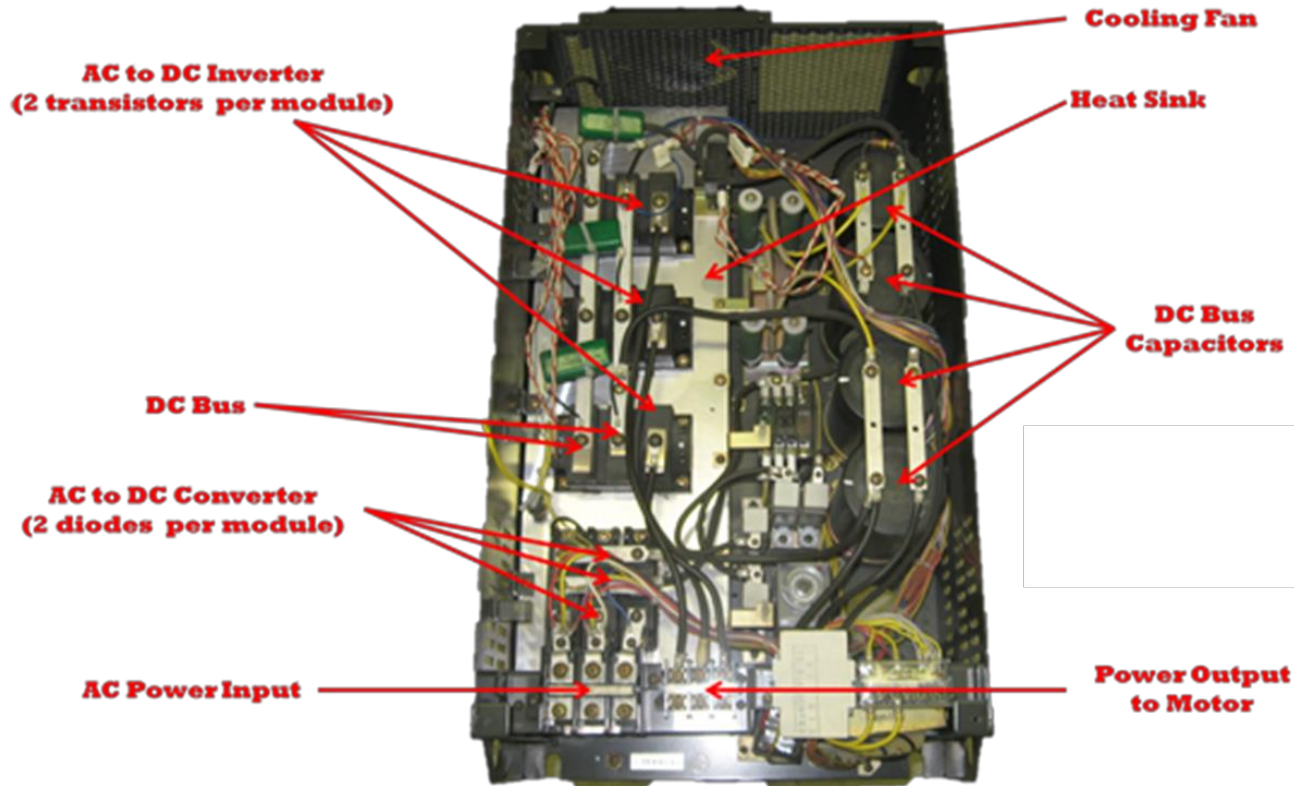


# An Actual AC Drive (VFD)

6

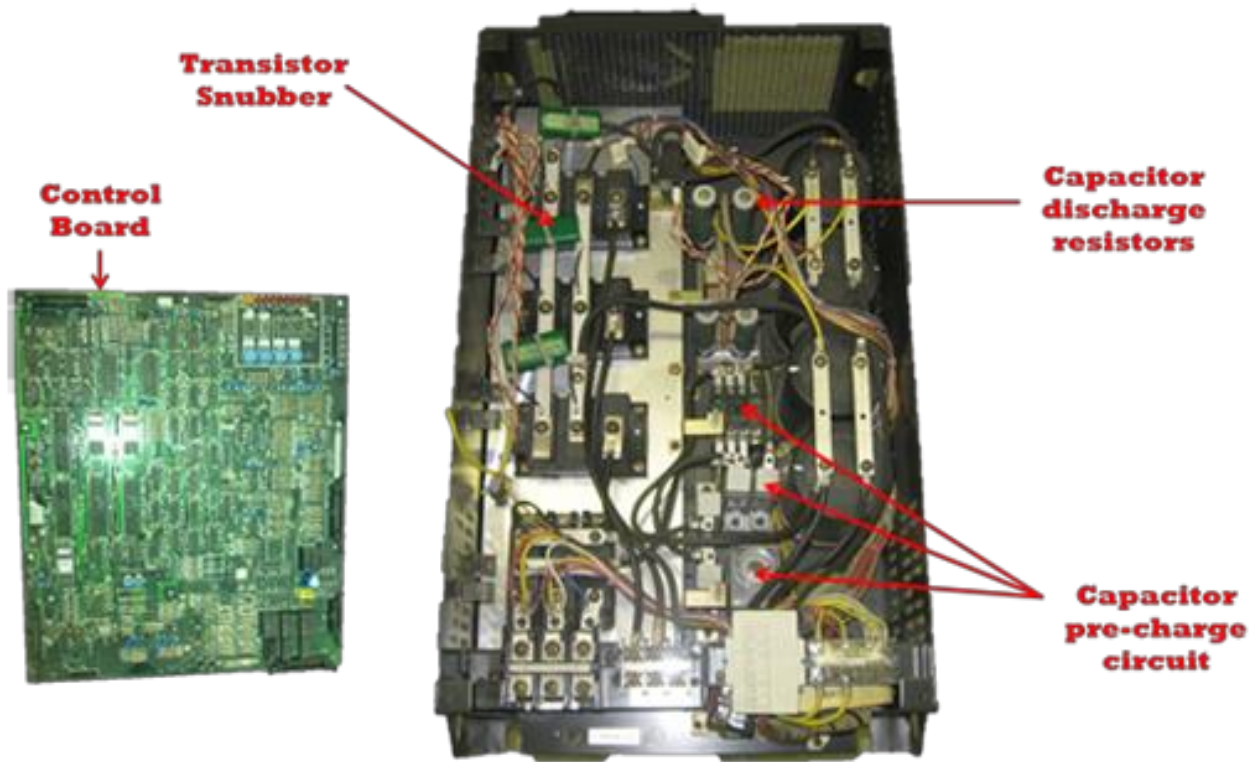

# Principle of an AC Drive

7


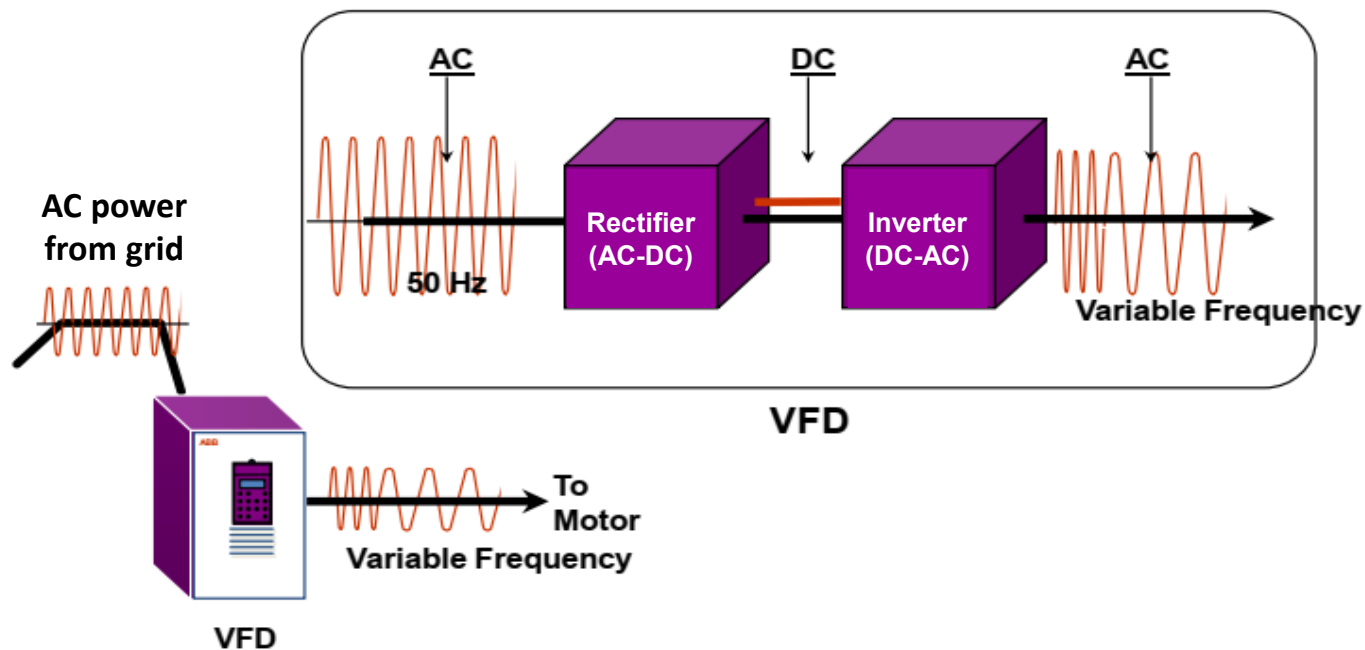


- First, the Converter (usually a diode **rectifier**) converts three-phase **AC power** (from grid or generator) to **DC power**.
- Next, the **DC Bus** stores and filters the **DC power** in a large bank of capacitors.
- Last, the **Inverter** (usually a set of six IGBTs) switches or **inverts** the **DC power** in a **Pulse Width Modulated (PWM) AC** waveform to the motor.

# Principle of an AC Drive

8

## 1<sup>st</sup> Stage: Rectifier

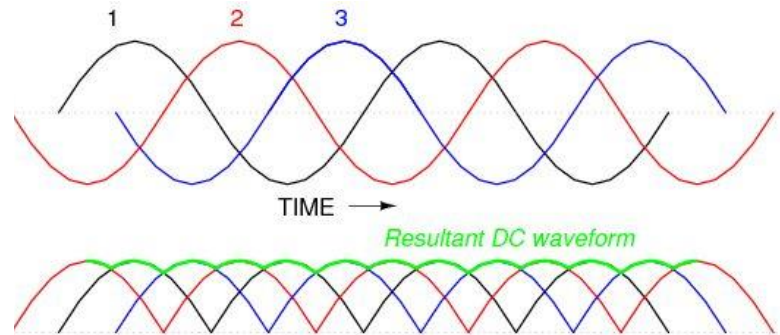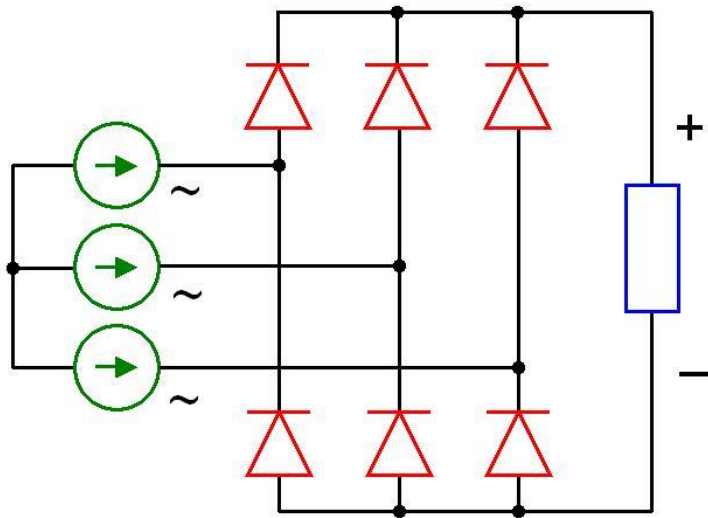




# Principle of an AC Drive


9

## 2<sup>nd</sup> Stage: DC Bus

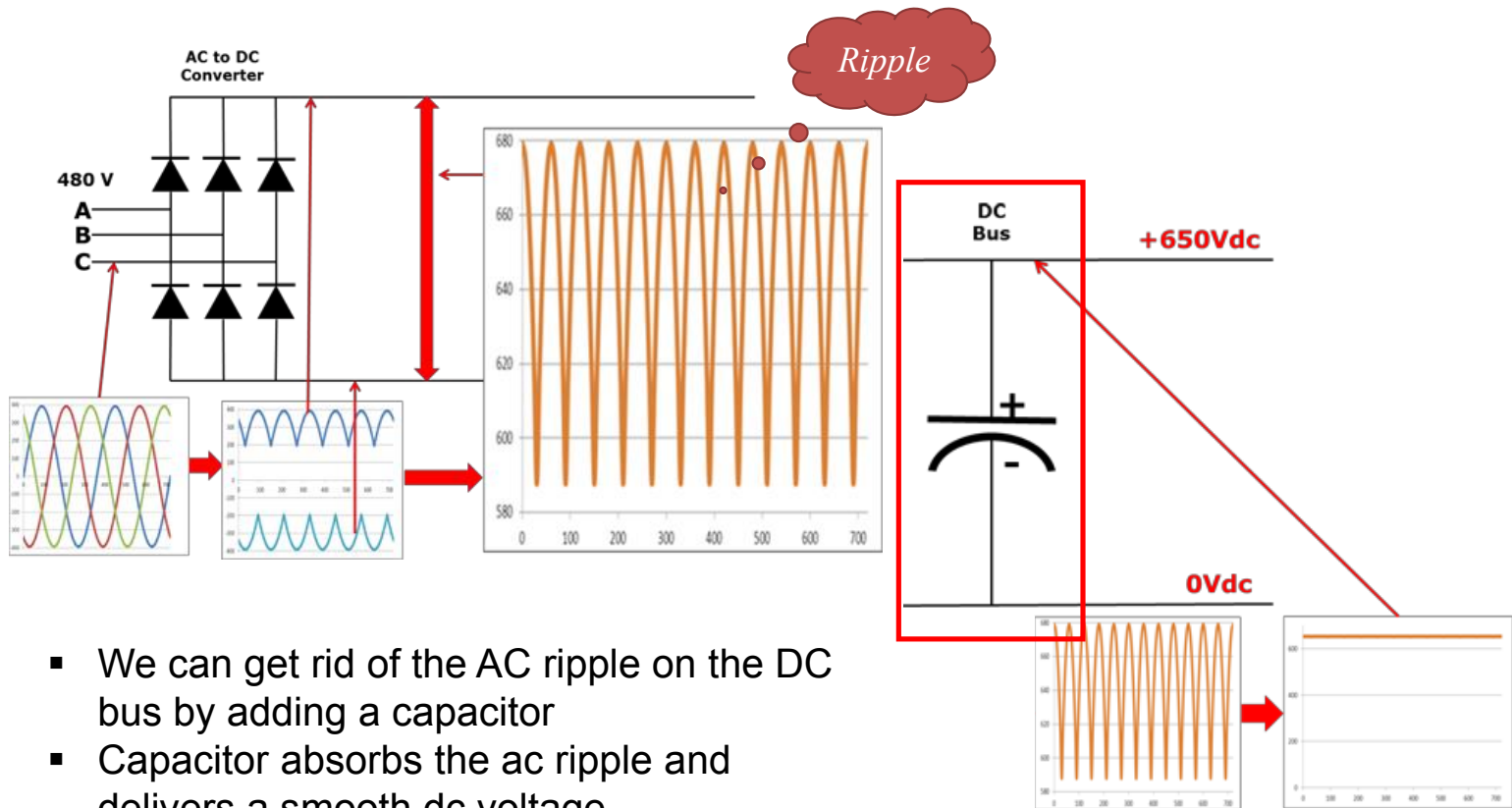


- We can get rid of the AC ripple on the DC bus by adding a capacitor
- Capacitor absorbs the ac ripple and delivers a smooth dc voltage.
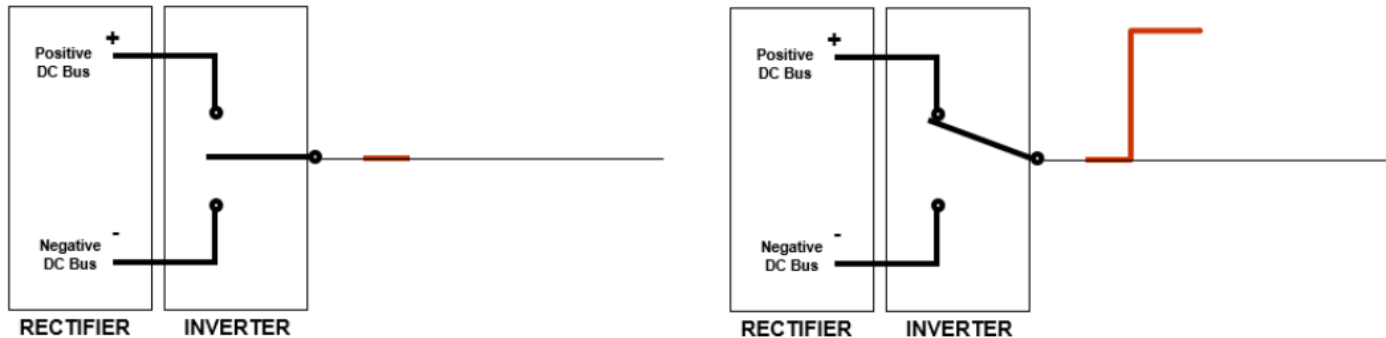
## 3<sup>rd</sup> Stage: Switching Sequence for converting DC to AC




- When we close one of the top switches in the inverter, that phase of the motor is connected to the positive dc bus and the voltage on that phase becomes positive

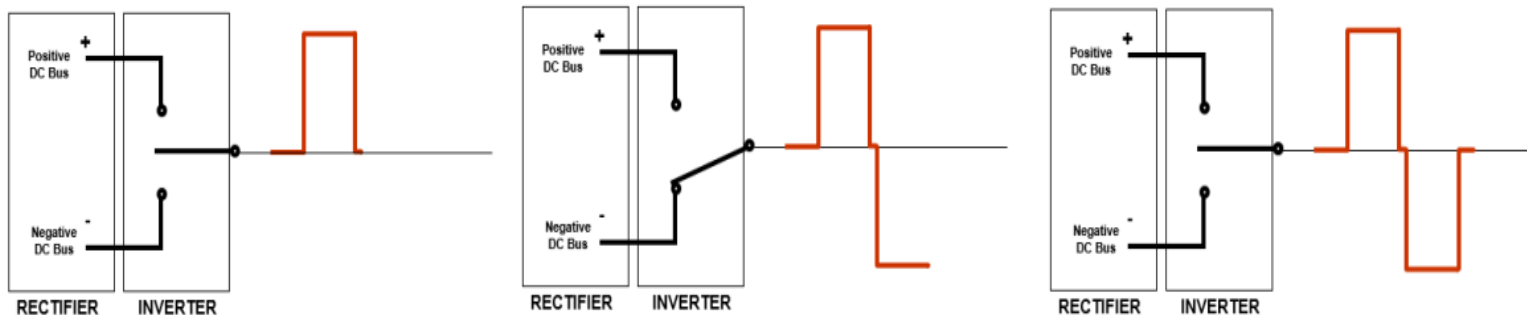
## 3<sup>rd</sup> Stage: Switching Sequence for converting DC to AC



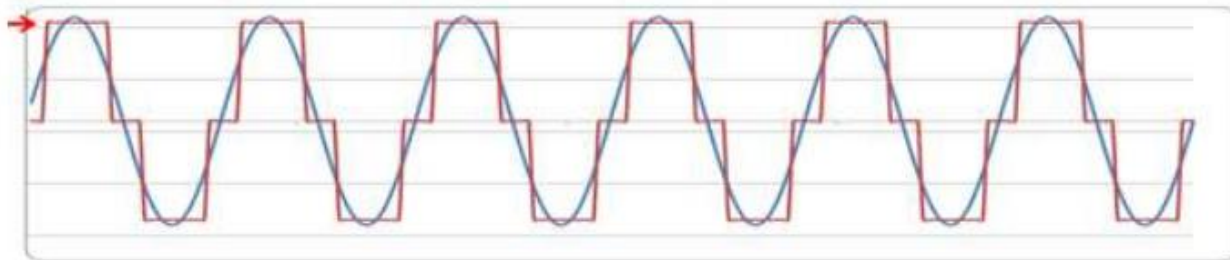- When we close one of the bottom switches in the converter, that phase is connected to the negative dc bus and becomes negative. Thus, we can make any phase on the motor become positive or negative at will and can thus generate any frequency that we want. So, we can make any phase be positive, negative, or zero.



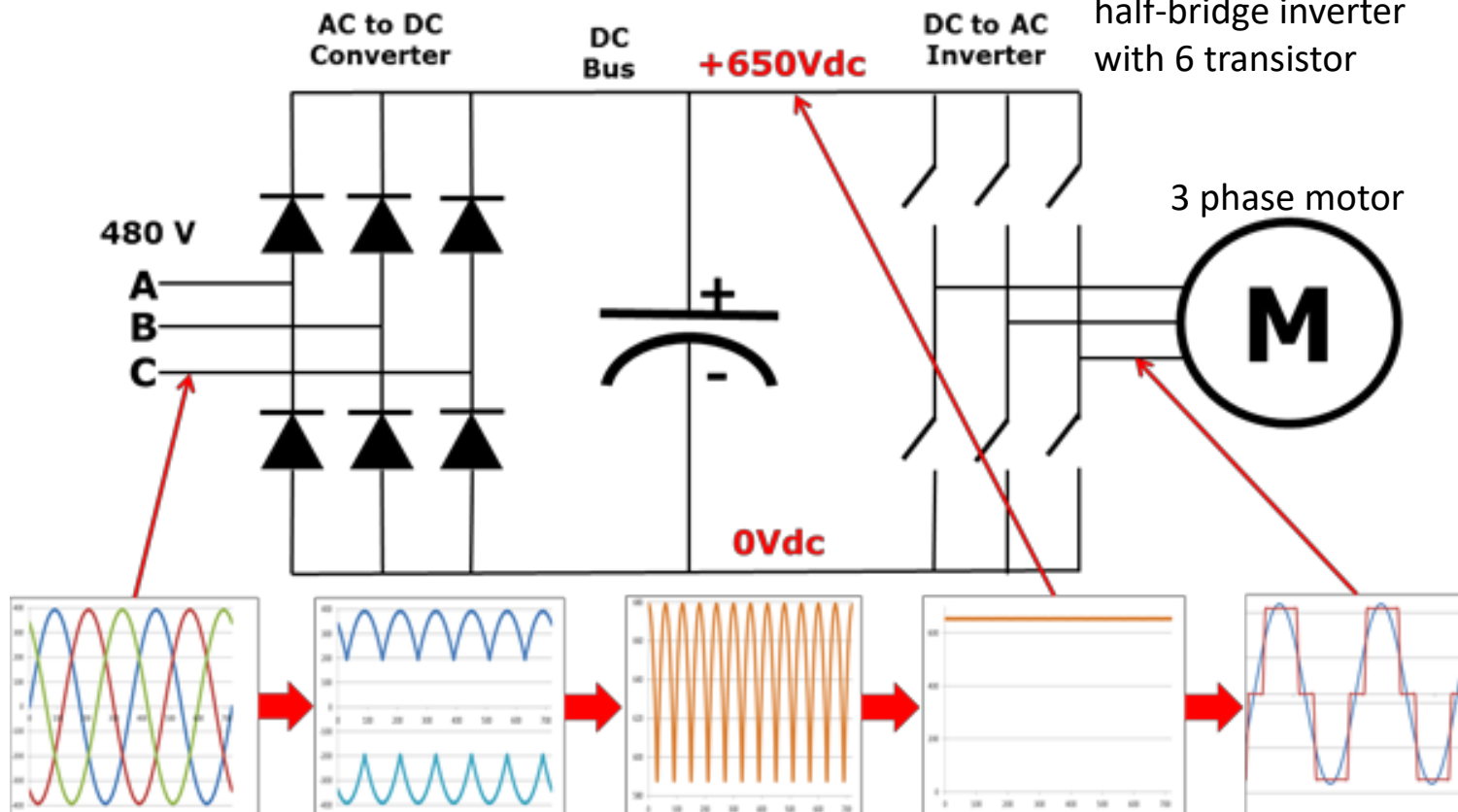This is a 3-phase half-bridge inverter with 6 transistor



- <https://www.vfds.com/blog/what-is-a-vfd>




成功大學

National Cheng Kung University


---

# Power Electronic Devices for Motor Drives


## DC to DC: CHOPPER

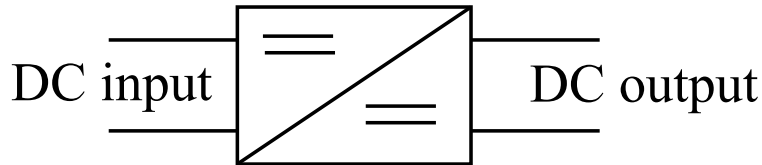


## AC to DC: RECTIFIER

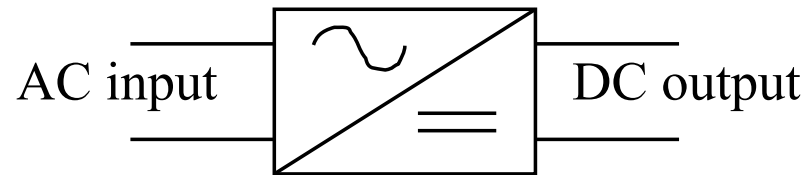

## DC to AC: INVERTER

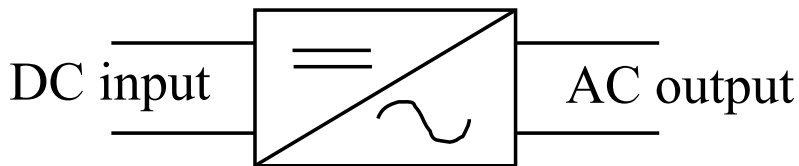

## AC to AC: CYCLO-CONVERTER

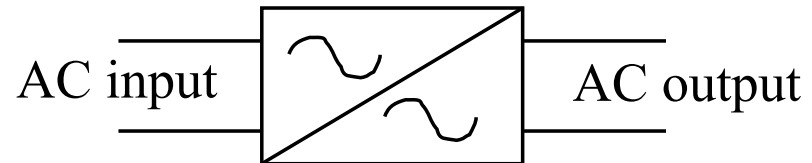

- Power semiconductor devices constitute the heart of modern power electronic apparatus. They are used in power electronic converters in the form of a matrix of on-off switches. and help to convert power from AC-to-DC (rectifier), DC-to-DC (chopper), DC-to-AC (inverter). and AC-to-AC at the same (ac controller) or different frequencies (cycloconverter).

## Diode

→ (Uncontrollable device)

*has only two terminals and can not be controlled by control signal.*

## Thyristor or Silicon-Controlled rectifier (SCR)

→ (Half-controllable device)

*is turned-on by a control signal and turned-off by the power circuit.*

*The on and off states of the device are controlled by control signals*



## MOSFET, IGBT, BJT, GTO

→ (Fully-controllable device)


*The on and off states of the device are determined by the power circuit.*
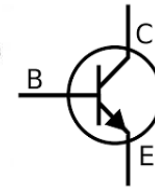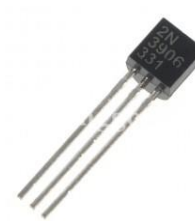
## Bipolar Junction Transistors (BJT)

As the **Bipolar Transistor** is a three terminal device, there are basically three possible ways to connect it within an electronic circuit with one terminal being common to both the input and output. Each method of connection responding differently to its input signal within a circuit as the static characteristics of the transistor vary with each circuit arrangement.




NPN  
Bipolar Junction  
Transistor

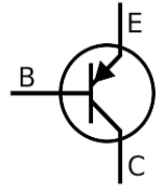



PNP  
Bipolar Junction  
Transistor

*Symbol*

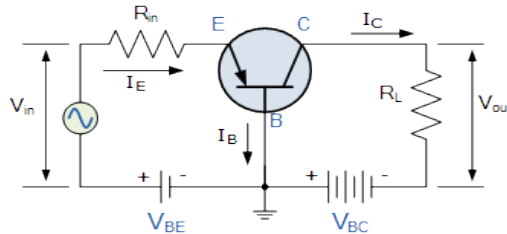**Common Base (CB)  
Transistor Circuit** –  
has Voltage Gain but  
no Current Gain.



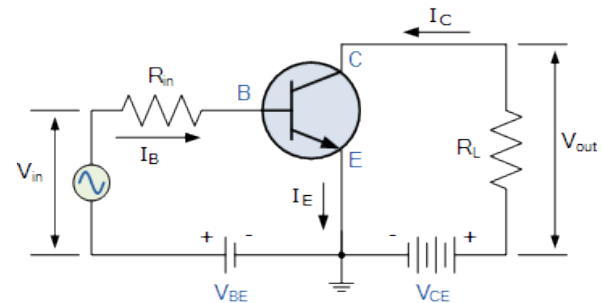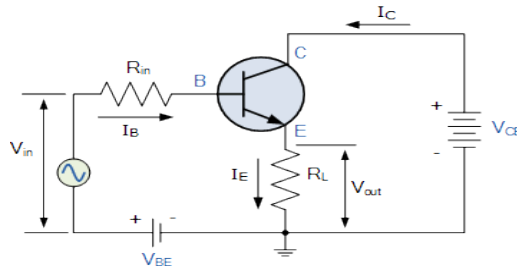**Common Collector  
(CC) Transistor Circuit**–  
has Current Gain but no  
Voltage Gain




**Common Emitter (CE) Amplifier Circuit** - has  
both Current and Voltage Gain

Available:

[https://www.electronics-tutorials.ws/transistor/tran\\_1.html](https://www.electronics-tutorials.ws/transistor/tran_1.html)



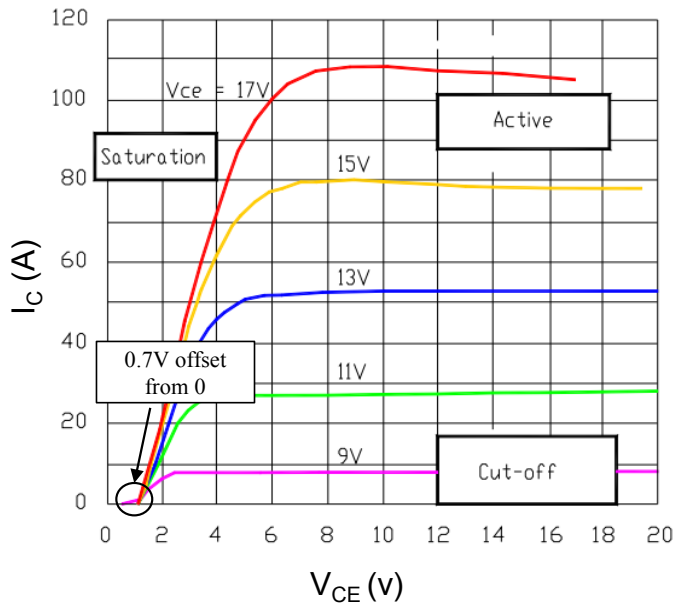
## Insulated Gate Bipolar Transistors (IGBTs)



Output  $I$ - $V$  characteristics of an NPT-IGBT [IXSH30N60B2D1].

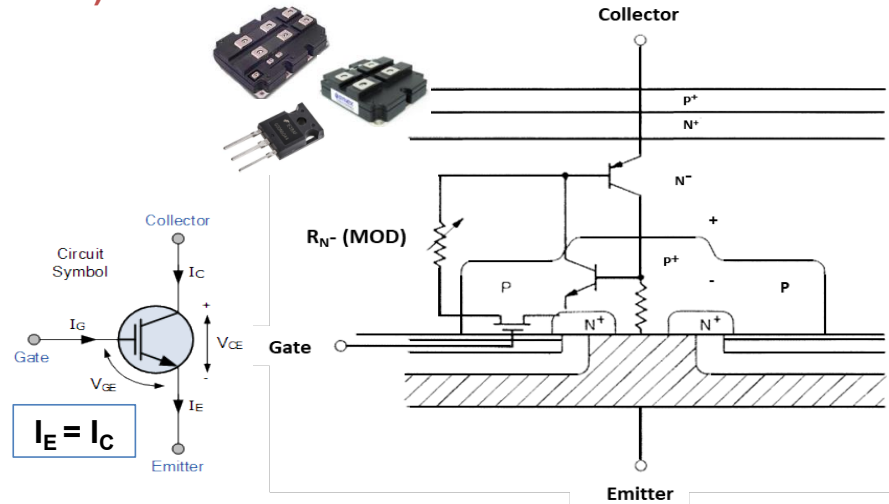The entire family of curves is translated from the origin by this voltage magnitude. It may be recalled that with a  $P^+$  collector, an extra  $P$ - $N$  junction has been incorporated in the IGBT structure.




Symbol

IGBT structure with equivalent circuit


This forward-biases the base-emitter junction of the  $P$ - $N$ - $P$  transistor, turning it on and causing conductivity modulation of the  $N$  legion. which gives a significant of conduction drop over that of a MOSFET. It is turned-off by reducing the gate voltage to zero or negative, which shuts off the conducting channel in  $P$  region.
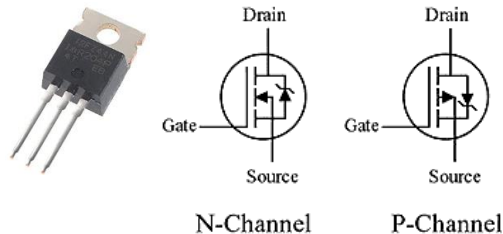
## Metal Oxide Semiconductor Field Effect Transistor (MOSFET)

MOSFETs use an electrical field produced by a gate voltage to alter the flow of charge carriers, electrons for n-channel or holes for P-channel, through the semi-conductive drain-source channel. The gate electrode is placed on top of a very thin insulating layer and there are a pair of small n-type regions just under the drain and source electrodes




*Symbol*

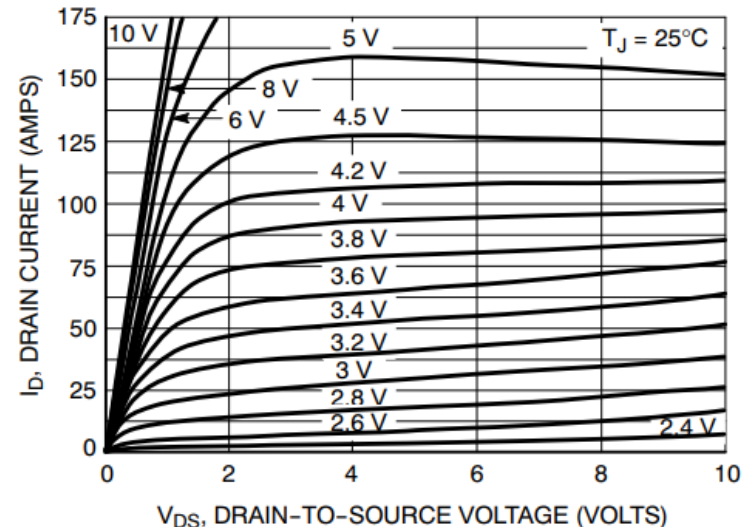


*I-V characteristics of an MOSFET [NTD70N033R]*

[https://www.electronics-tutorials.ws/transistor/tran\\_6.html](https://www.electronics-tutorials.ws/transistor/tran_6.html)
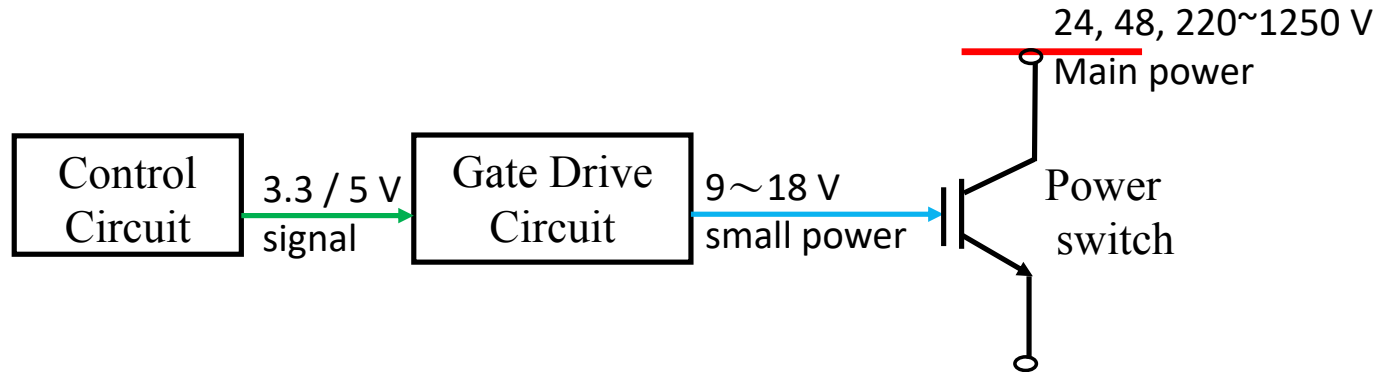
<http://www.onsemi.com/pub/Collateral/NTD70N03R-D.PDF>



- Interface between control (low power electronics) and (high power) switch.
- Functions:
  - **Amplification:** amplifies control signal to a level required to drive power switch
  - **Isolation:** provides electrical isolation between power switch and logic level
- Complexity of driver varies markedly among switches.
  - MOSFET/IGBT drivers are simple
  - BJT drivers are very complicated and expensive.

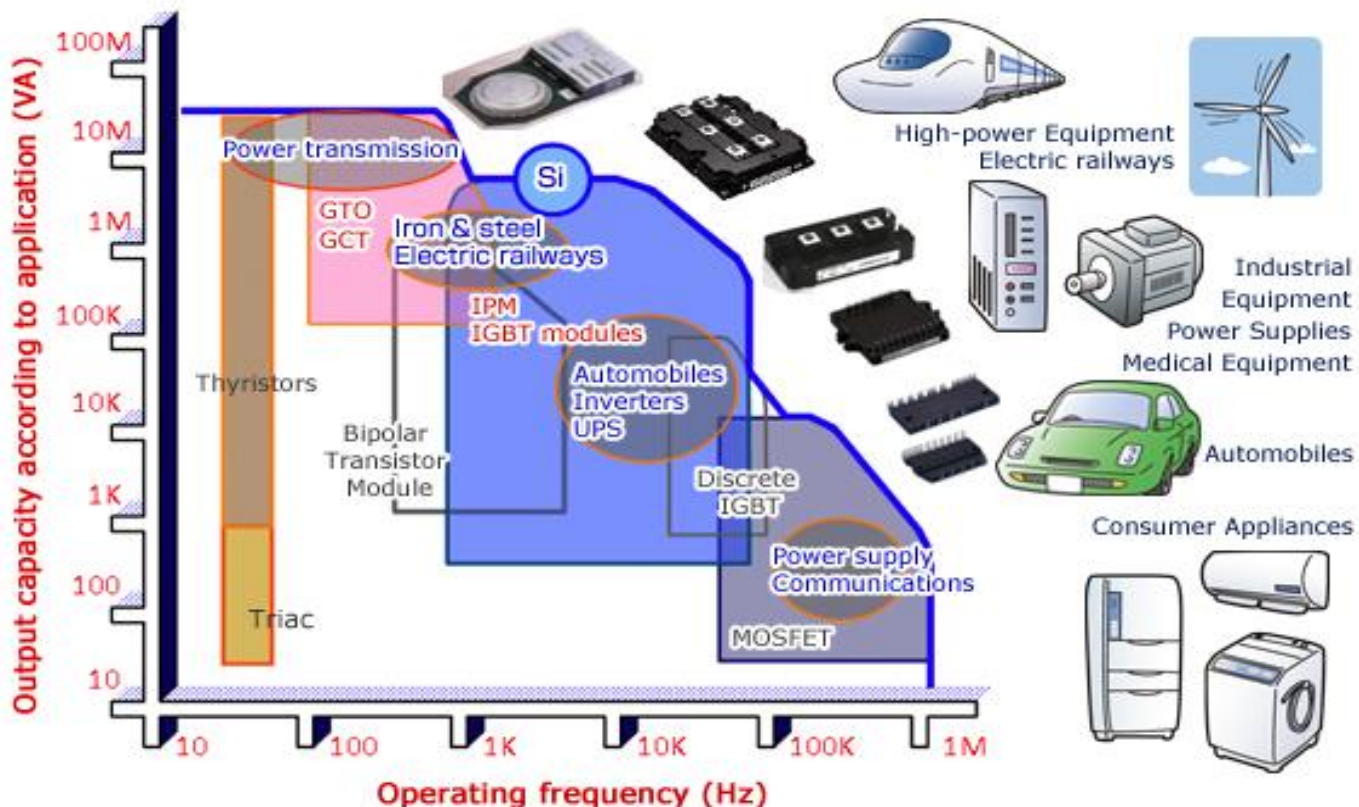

Currently, the majority of the development in power electronics applied in the area of mid- to high-power conversion is sustained by the evolving IGBT and IPM technologies.


[http://www.mitsubishielectric.com/semiconductors/triple\\_a\\_plus/technology/01/index.html](http://www.mitsubishielectric.com/semiconductors/triple_a_plus/technology/01/index.html)

Characteristic	BJT	MOSFET	IGBT	SiC MOSFET
Voltage rating	High <1kV	High <1kV	Very High>1kV	Very High>1kV
Current rating	High	Low	High	Medium
Input Drive	Current $h_{FE}$ 20-200	Voltage $V_{GS}$ 3-10V	Voltage $V_{GE}$ 4-8V	Voltage $V_{GS}$ 15-18V
Input Impedance	Low	High	High	High
Output Impedance	Low	Medium	Low	Low
Switching speed	Slow	Fast	Medium	Very Fast
Cost	Low	Medium	Medium	High

Available: <https://www.electronics-tutorials.ws/power/insulated-gate-bipolar-transistor.html>


Wide-band gap (WBG) devices use materials such as silicon carbide (SiC) or gallium nitride (GaN) that are different from silicon-based (Si) component and have unique physical parameter.

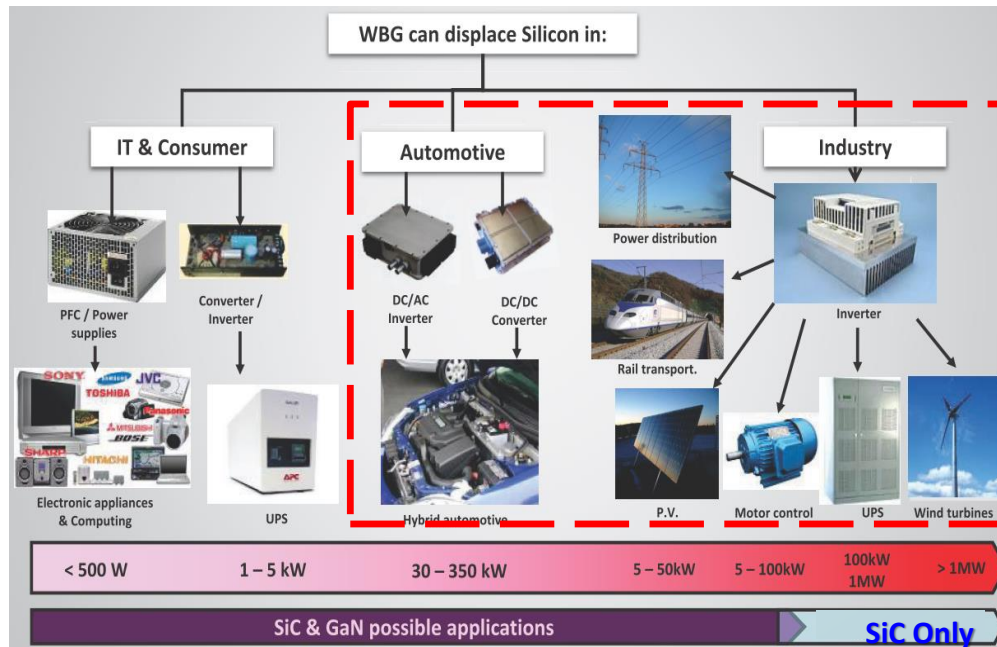The wide energy gap is characterized by a larger energy difference than Si in the conduction band, enabling them to switch on and off more quickly.



Ref : Yole Développement, Market & Technology trends in Wide BandGap power packaging, 2015

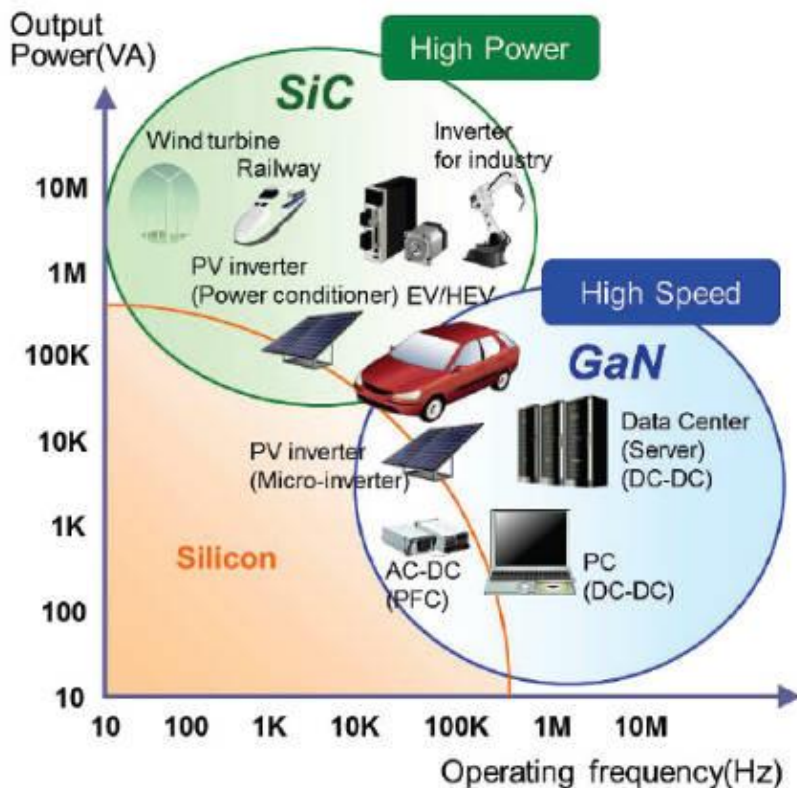SiC fits high power demand and higher temperature environment such as motor with built-in drives for electric vehicles and applications.




**SiC** for high power voltages ( $>1\text{kV}$ ) with high current  
= niche market


**GaN on Si** for high frequency at midrange voltages ( $<1\text{kV}$ , up to  $100\text{A}$ )  
= mass market

<https://uk.tek.com/blog/look-back-apec-thoughts-gan-products>

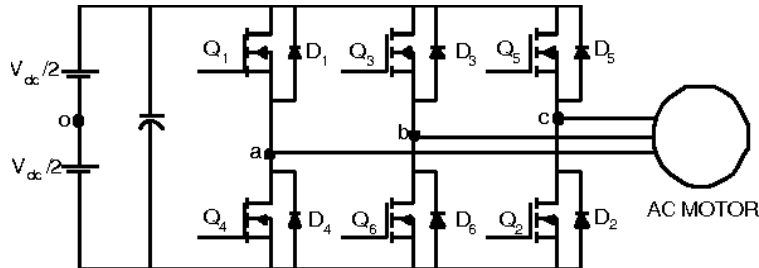
## Example: Effect of Silicon Carbide (SiC) Power Devices



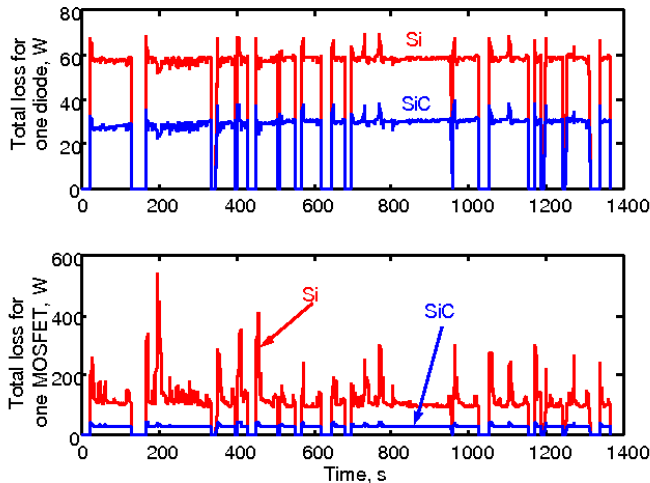Burak Ozpineci, Leon M. Tolbert, Syed Kamrul Islam,  
*"Effects of Silicon Carbide ( SiC ) Power Devices on  
 HEV PWM Inverter Losses", 27th Annual Conference  
 of the IEEE Industrial Electronics Society , 2001*



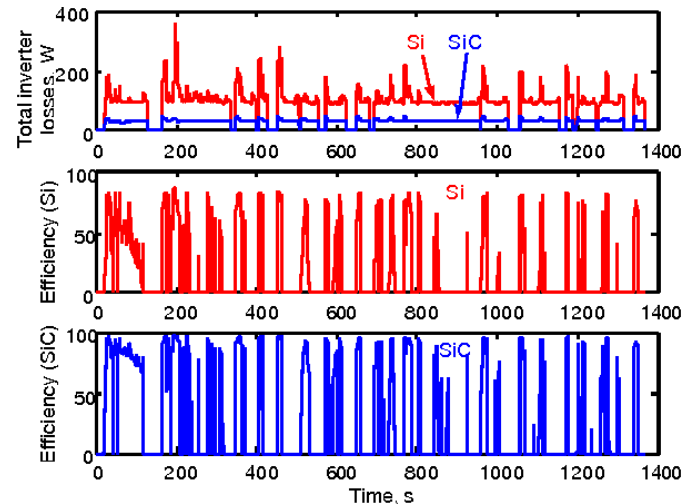Total losses of each MOSFET and diode over the FUDS cycle (Si-red, top, and 4H-SiC-blue)



Total losses and the efficiency of the inverter over the FUDS cycle (Si-red, top, and 4H-SiC-blue)





成功大學


National Cheng Kung University<sup>25</sup>

---

# Motor control method and drive circuit


Brushless motor controls the steering, speed, and torque by adjusting the voltage combination of each phase in the drive circuit.

## Synchronous PM Motor Drive

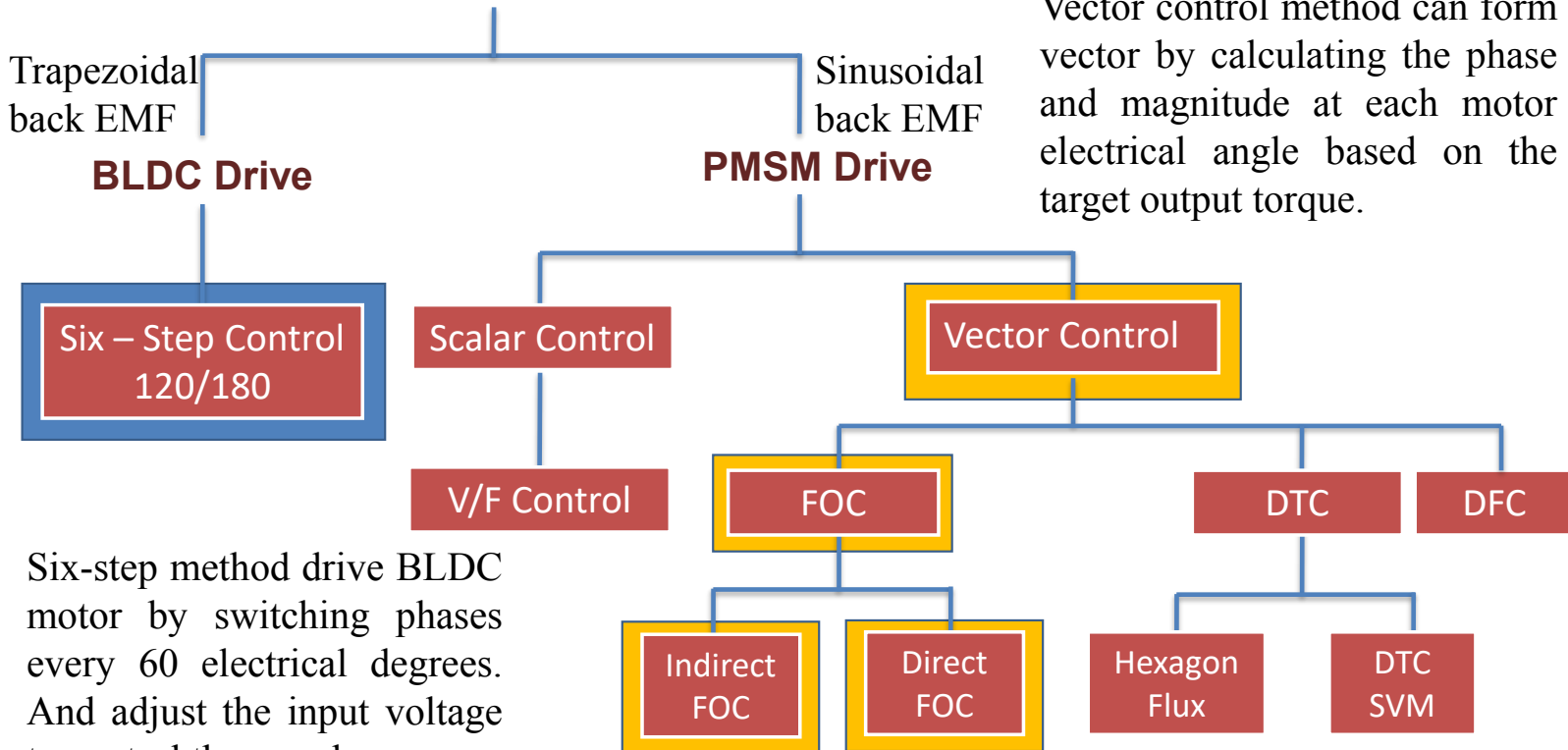


Six-step method drive BLDC motor by switching phases every 60 electrical degrees. And adjust the input voltage to control the speed.

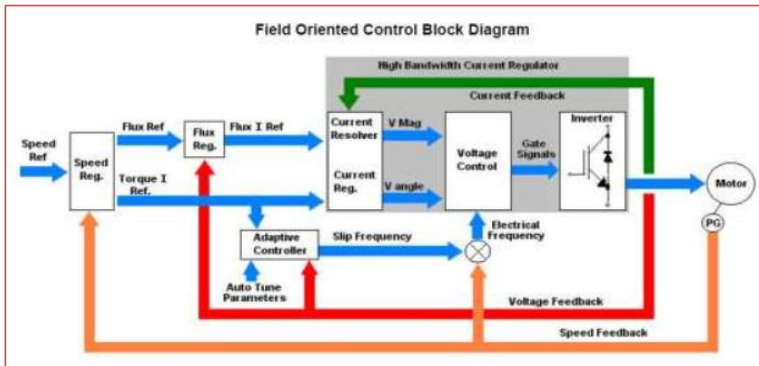- More Accurate than V/f Control.
- There are 2 types
  - Sensored FOC
  - Sensorless FOC



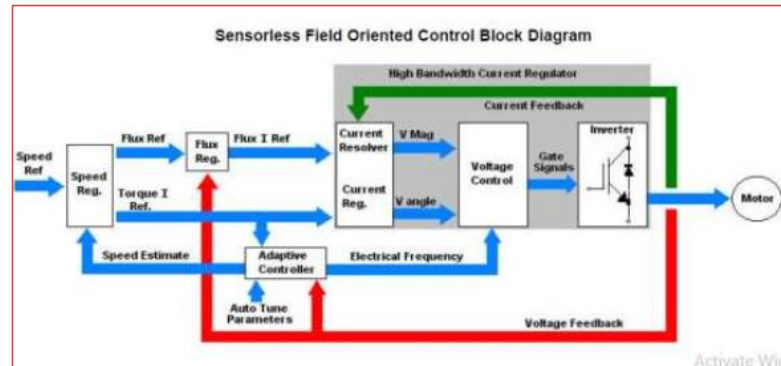- Feedback through position sensor
- Better speed regulations up to 0.01%
- Faster response to load variations





- No feedback through position sensor
- Feedback is derived through motor terminals
- Drive need to go through “Auto tuning”
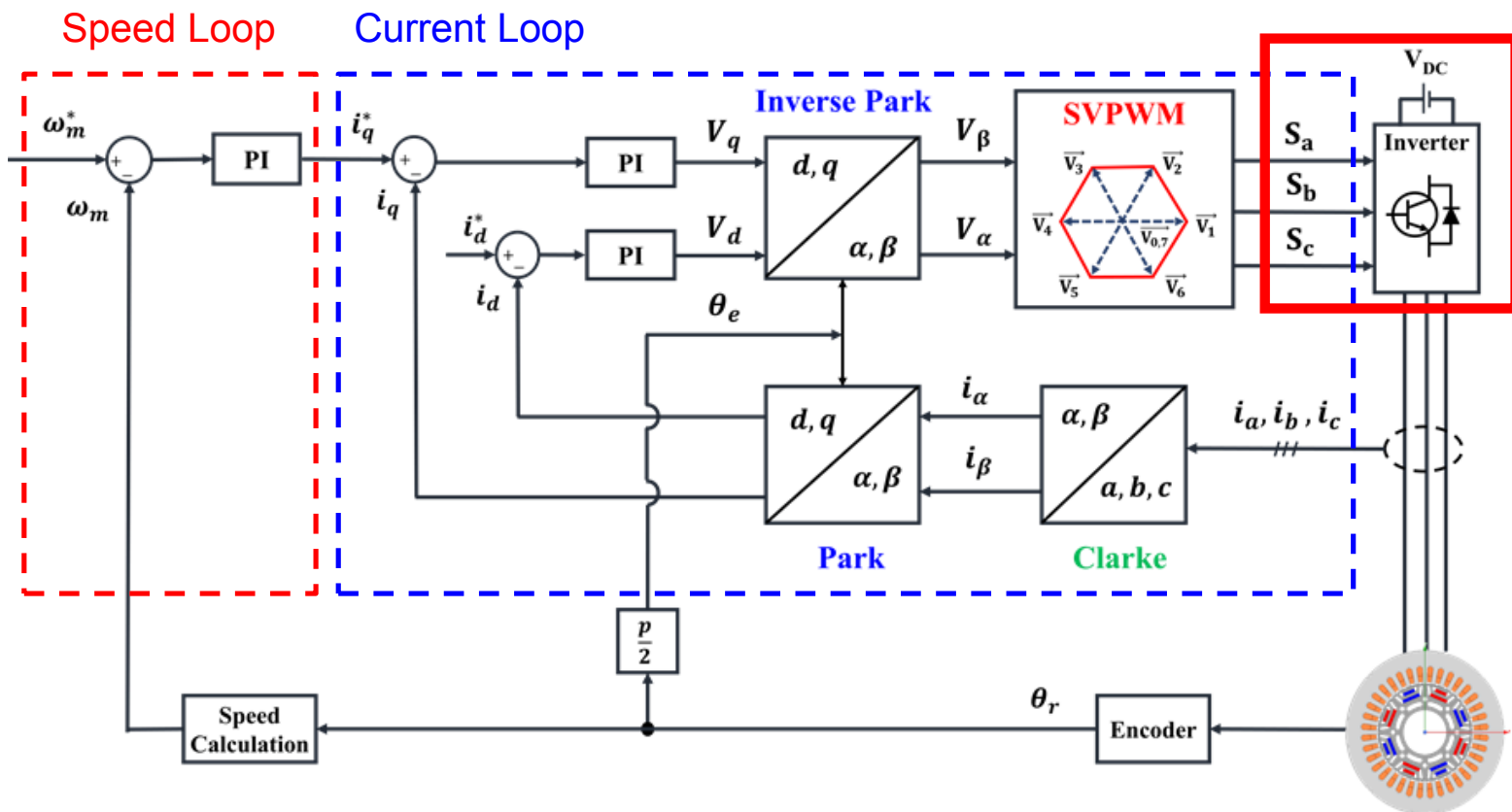
# Control Architecture of FOC for PMSM

28

The motor drive circuit is the INVERTER part on the right side of the control block figure below. Which receives switch commands and transmits energy to the motor.



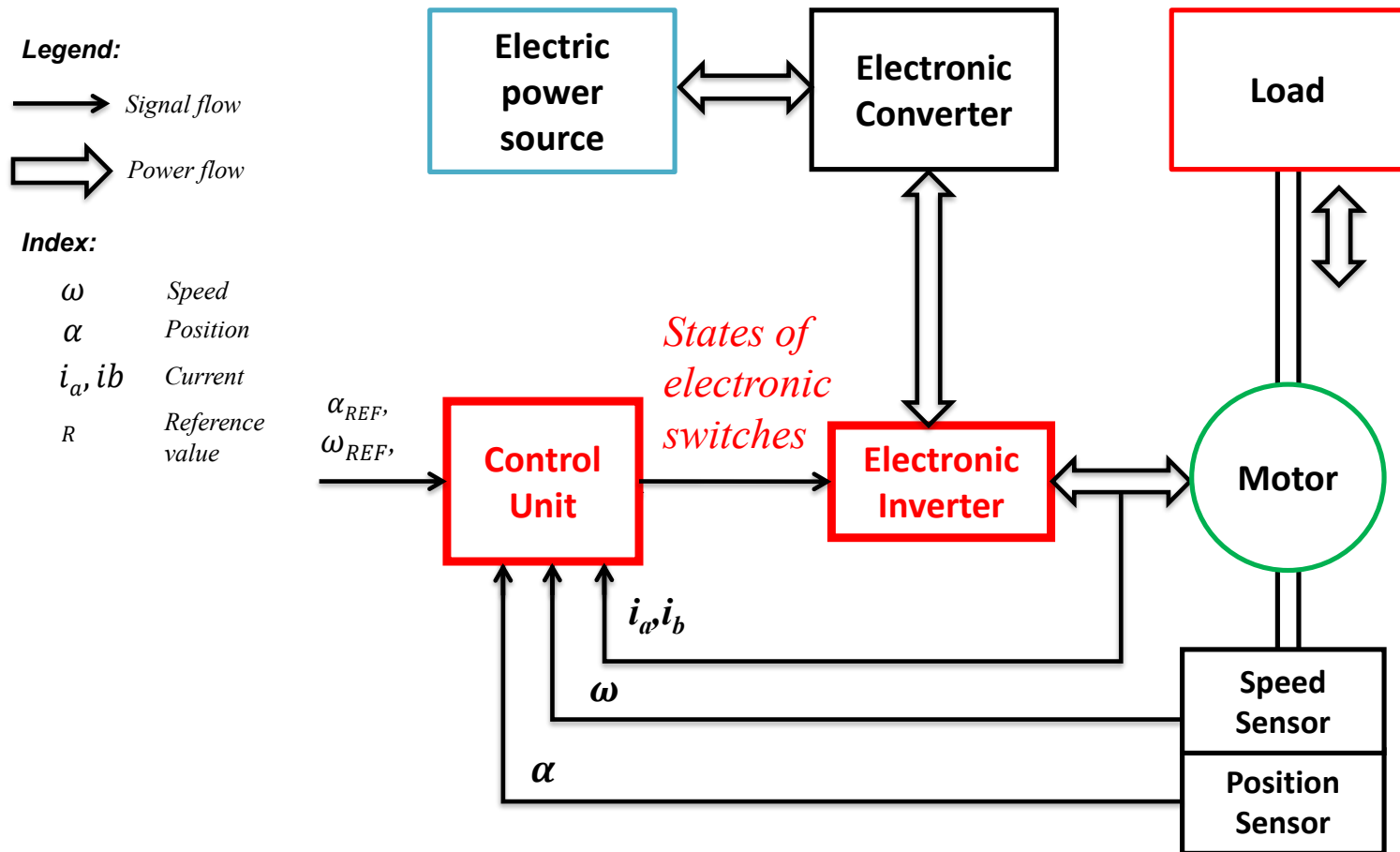



成功大學

National Cheng Kung University <sup>30</sup>


---

# Pulse Width Modulation

- The electrical converter and inverter blocks on the previous page are used to control the high voltage output with digital signals.
- When they work, DC voltage for power is continuously switched by the transistor with control signal, and the voltage transfer to a series of square wave pulses.
- By controlling the proportion of the turn-on-time of the pulse, called the duty ratio, its output can be adjusted as the equivalent voltage during long-term operation.
- This method is called **pulse width modulation (PWM)**, where the pulse has switching frequency, and width is the length of time that square wave is on refer to duty.
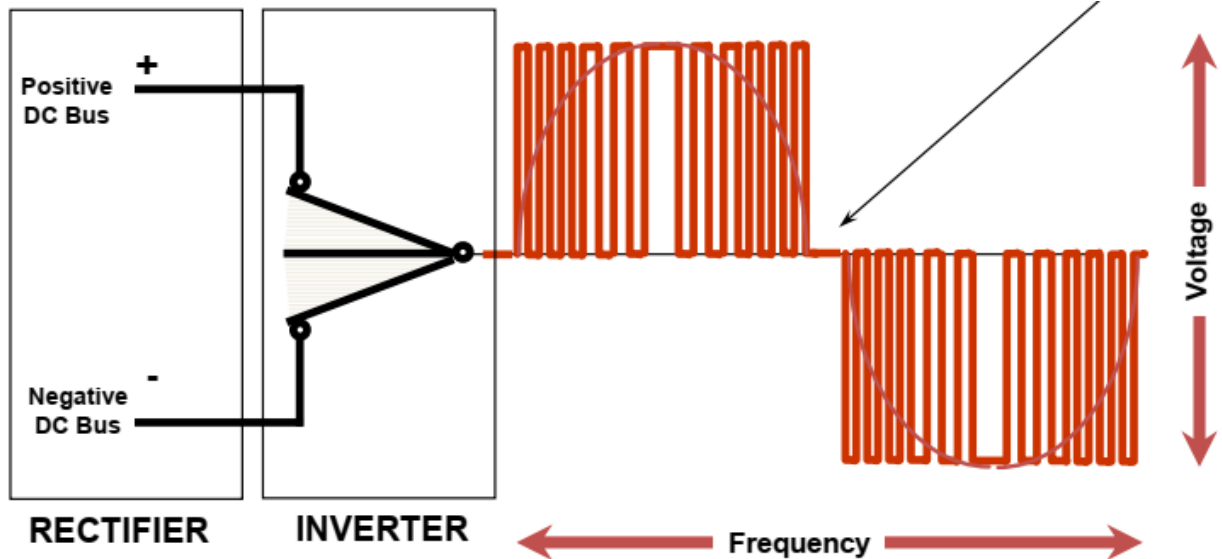
## Pulse Width Modulation

How often you switch from positive pulses to negative pulses determines the frequency of the waveform






- The basic principle of PWM can be stated that under constant supply voltage  $V_{DC}$ , when voltage is applied to the resistance load in pulses. The instantaneous output voltage  $v_o$  is determined:

$$V_0 = \frac{T_{ON}}{T_{ON} + T_{OFF}} V_{DC}$$


- The voltage applied to the load can thus be changed using the time duty-cycle ratio

$$W = \frac{T_{ON}}{T_{ON} + T_{OFF}}$$

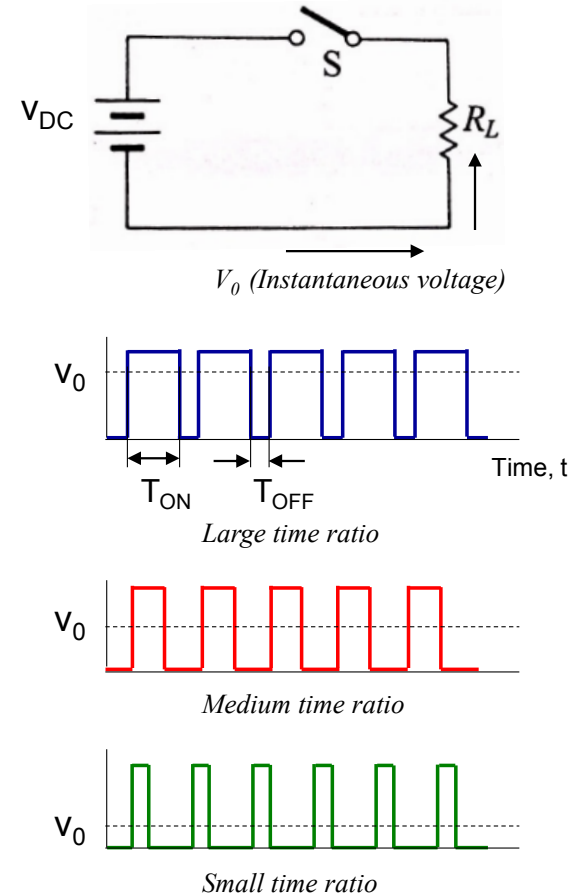**Pulses with fixed frequency and magnitude but variable width**



Trapezoidal back EMF

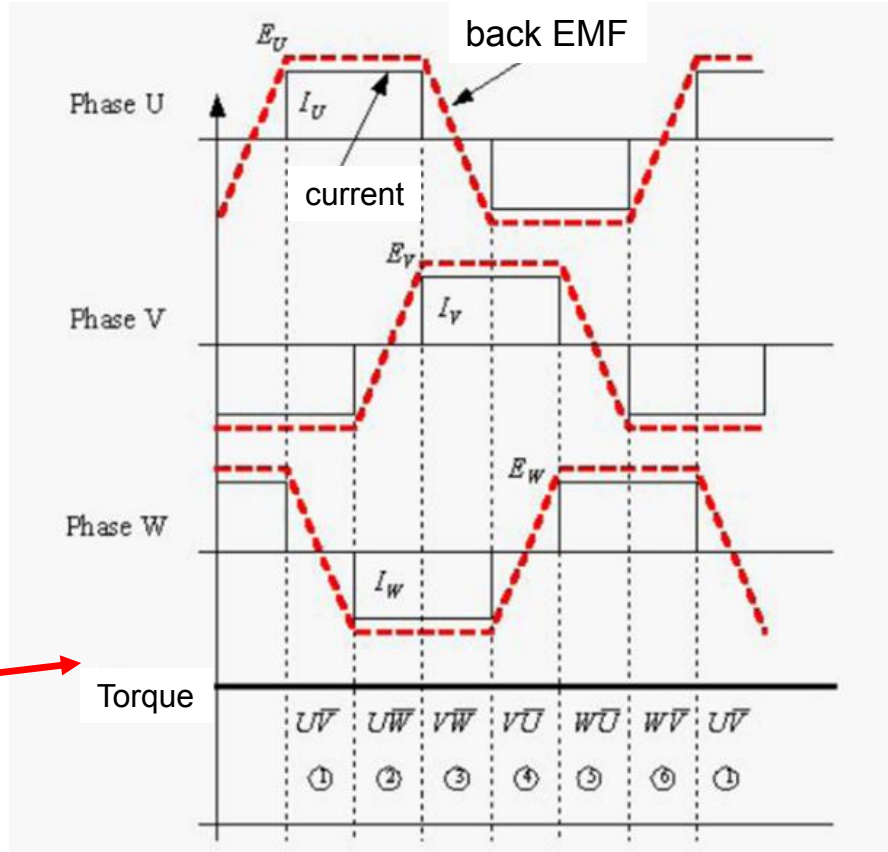


**Ideal condition**

Torque


$$T = k_{E_U} \cdot i_U + k_{E_V} \cdot i_V + k_{E_W} \cdot i_W$$

$$= 2K_E I$$

Sinusoidal back EMF




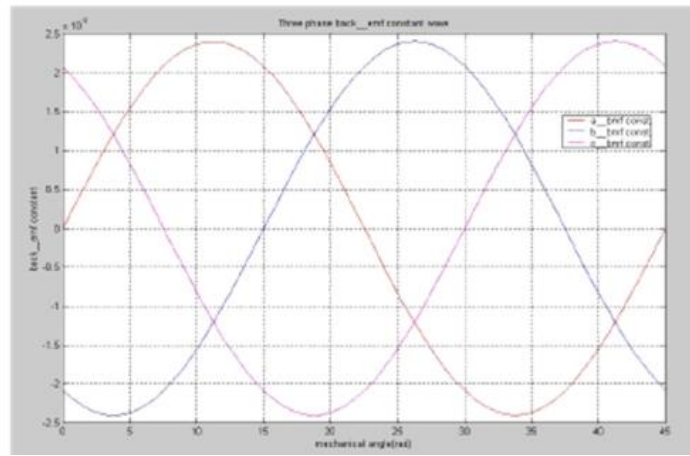


Three-phase sinusoidal wave current

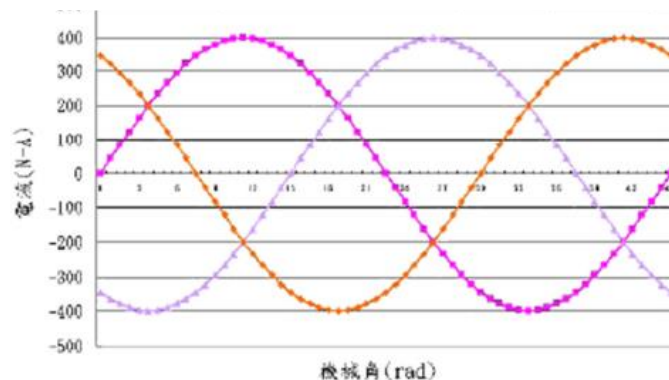

$$\begin{aligned} T &= k_{eA} \cdot i_A + k_{eB} \cdot i_B + k_{eC} \cdot i_C \\ &= K_e \cdot \sin\theta \cdot I \sin\theta + \\ &\quad K_e \cdot \sin(\theta - 120^\circ) \cdot I \sin(\theta - 120^\circ) + \\ &\quad K_e \cdot \sin(\theta + 120^\circ) \cdot I \sin(\theta + 120^\circ) \\ &= K_e \cdot I \cdot \{ \sin^2\theta + \sin^2(\theta - 120^\circ) \\ &\quad + \sin^2(\theta + 120^\circ) \} \\ &= \frac{3}{2} K_e I \end{aligned}$$

- Space vector modulation (SVM) is an algorithm for the control of pulse width modulation (PWM). It is used for the creation of alternating current (AC) waveforms; most commonly to drive 3 phase AC powered motors at varying speeds from DC using multiple class-D amplifiers. There are variations of SVM that result in different quality and computational requirements. One active area of development is in the reduction of total harmonic distortion (THD) created by the rapid switching inherent to these algorithms.

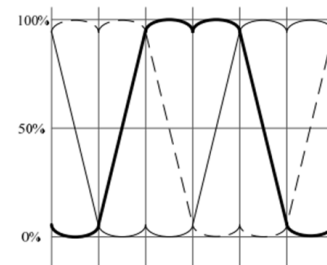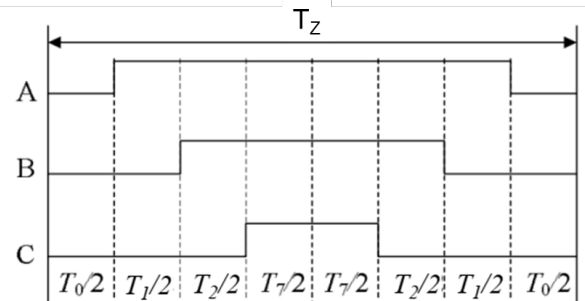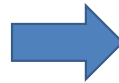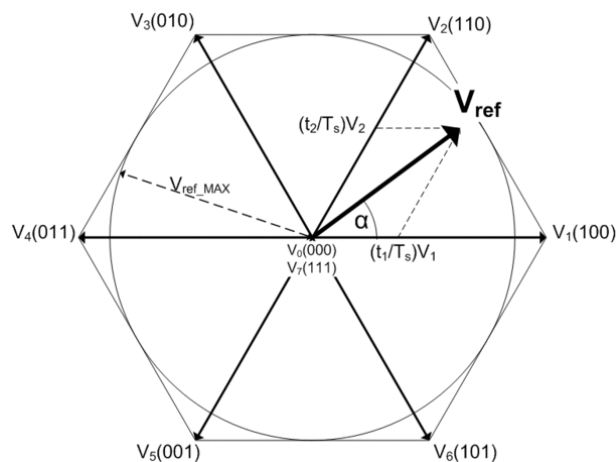

- [https://en.wikipedia.org/wiki/Space\\_vector\\_modulation](https://en.wikipedia.org/wiki/Space_vector_modulation)